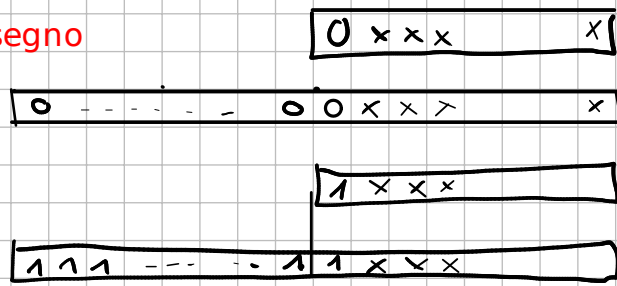


estensione del segno



LOGICA BOOLEANA

AND congiunzione
 — 2 ingressi (n)

OR disgiunzione

NOT negazione
 1 ingresso

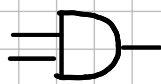


TABELLE VERITÀ

Ingressi	uscite
----------	--------

conf. ingressi

conf. delle uscite

AND

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

2^m

OR

x	y	z
0	0	0
0	1	1
1	0	1
1	1	1

x	z
0	1
1	0

f : 4bit → # "1"

a	b	c	d	z ₁	z ₂	z ₃
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	0
0	1	1	1	0	1	1
...
1	1	1	1	1	0	0

f[16]

f[0] = 0
 f[1] = 1
 f[2] = 1
 f[3] = 2


$z_1 = a \text{ AND } b \text{ AND } c \text{ AND } d$

AND


OR +

$z_2 = \bar{a} \text{ AND } \bar{b} \text{ AND } c \text{ AND } d$

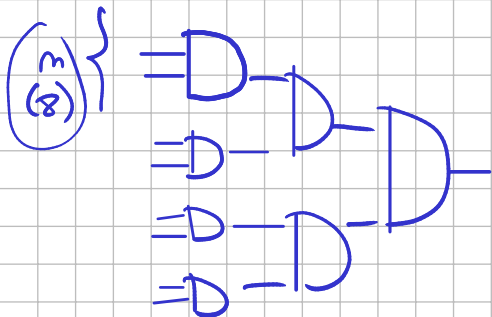$z_2 = \bar{a}\bar{b}cd + \bar{a}b\bar{c}d + \bar{a}bc\bar{d} + \bar{a}bcd +$


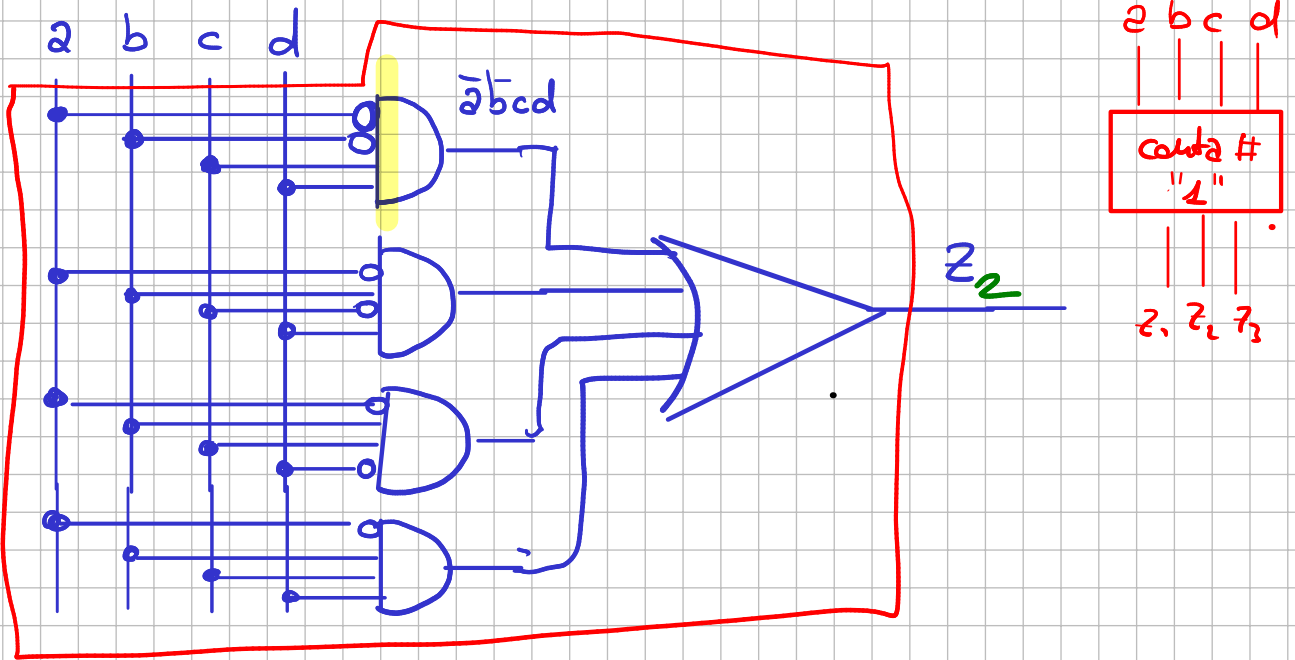
$$z_2 = \bar{a}\bar{b}cd + \bar{a}b\bar{c}d + \bar{a}bcd + a\bar{b}cd +$$



g: n° de 4 bit, n° de 4 bit → Données

$x_1 x_2 x_3 x_4$	$y_1 y_2 y_3 y_4$	c	$z_1 z_2 z_3 z_4$
0			0
1			1
0			0
1			1
1			1
1			1
1			1
1			1

256
règles

$$z_1 = \dots + \dots + \dots + \dots$$



a	b	z
0	0	0
0	1	1
1	0	1
1	1	1

$$z = \bar{a}b + a\bar{b} + ab$$

$$z = \bar{a}b$$

00
11



0
1

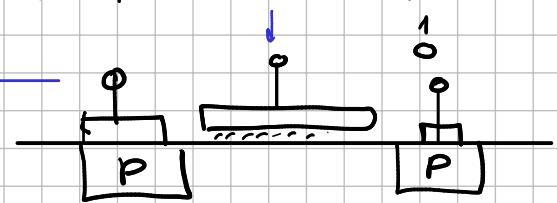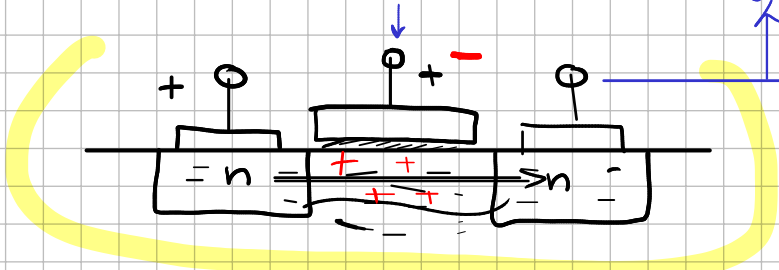


transistor n mos



p-mos

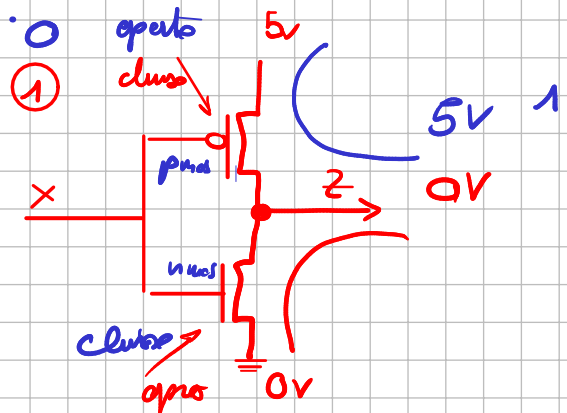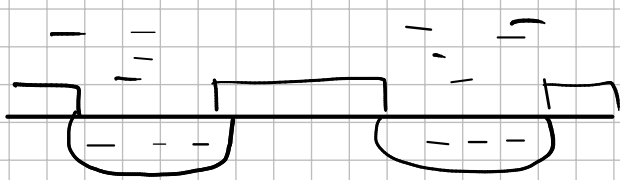

Sommatare

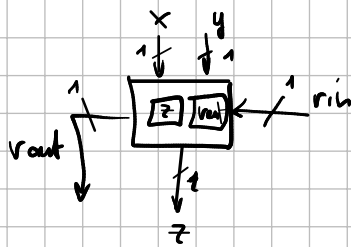

x	y	rin	z	rout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$z = \bar{x}\bar{y}rin + \bar{x}y\bar{rin} + x\bar{y}\bar{rin} + xy\bar{rin}$$

$$rout = \bar{x}y\bar{rin} + x\bar{y}rin + xy\bar{rin} + xyrin$$

arbitro

4 richieste

1 ack

16
rifer

r ₁	r ₂	r ₃	r ₄	a ₁	a ₂	a ₃	a ₄
1	-	-	-	1	0	0	0
0	1	-	-	0	1	0	0
0	0	1	-	0	0	1	0
0	0	0	1	0	0	0	1
0	0	0	0	0	0	0	0

$$a_1 = r_1$$

$$a_2 = \bar{r}_1 r_2$$

$$a_3 = \bar{r}_1 \bar{r}_2 r_3$$

$$a_4 = \bar{r}_1 \bar{r}_2 \bar{r}_3 r_4$$

	Volere	valore
_____	1	1
_____	1	1
_____	0	1

valore =

$\{0, 1\}$

AND OR NOT
 \cdot $+$ $\overline{\quad}$
 \times

identiti

↓

$$B \cdot 1 = B$$

$$B + 0 = B$$

$$B \cdot B = B$$


$$B + B = B$$

$$A \cdot B = B \cdot A \quad A + B = B + A$$

$$(A + B) + C = A + (B + C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$
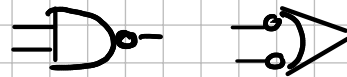
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$



funzione (descrizione)

↓
Tab Verità

testi addizionali: quanti sono gli 1 nella colonna delle uscite
 tante righe quanti sono gli ingressi


↓
Somme di prodotti

$$z = \overline{x} \overline{y} r_{in} + \overline{x} y r_{in} + x \overline{y} \overline{r_{in}} + x y r_{in}$$

$$r_{out} = \overline{x} y r_{in} + x \overline{y} r_{in} + x y r_{in}$$

$$r_{out} = y r_{in} + x \overline{y} r_{in} + x y r_{in}$$
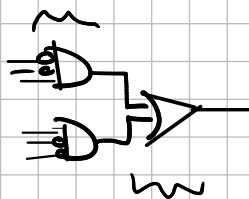
$$\overline{x} \overline{y} r_{in} + x \overline{y} r_{in}$$



$$\overline{y} (\overline{x} r_{in} + x r_{in})$$

$$y r_{in} (\overline{x} + x)$$

$$y r_{in} \cdot 1$$

$$y r_{in}$$

$$\overline{y} (\overline{x} r_{in} + x r_{in})$$

